Chapter 1 DC Circuit Analysis

In the most basic circuit, you have only a battery and a resistor:



In this case, you only need Ohm's Law: V = IR. In this case, $6V = 3\Omega \times 2A$.

Exercise 1 Ohm's Law



How many amps are going around the circuit?



1.1 Resistors in Series

When you have two resistors wired together in a long line, we say they are "in series". If you have two resistors R_1 and R_2 wired in series, the total resistance is $R_1 + R_2$.

In this diagram, for example, the total resistance is 5Ω .



The current flowing through the circuit, then, is 10/4 = 2A.

By Ohm's law, the voltage drop across the upper resistor is $IR = 2A \times 3\Omega = 6V$.

The voltage drop across the lower resistor is $IR = 2A \times 2\Omega = 4V$.

Notice that the battery pumps the voltage up to 10V, then the two resistors drop it by exactly 10V. This is known as "Kirchhoff's Voltage Law":

Kirchhoff's Voltage Law

As you make a loop around a circuit, the sum of the voltage increase must equal the sum of the voltage decrease.

The negative end of the battery is connected to "ground" (it has zero voltage), then we can draw a diagram with the voltages(That symbol in the lower right represents a connection to ground).



Exercise 2 Resistors In Series

Working Space

What is the current going around the circuit?

What is the voltage drop across each resistor?



1.2 Resistors in Parallel

Look at this circuit. Note that the current can go two different paths.



There is 12 volts pushing current through both resistors. So 6A will go through the 2Ω resistor and 4A will go through the 3Ω resistor.



Thus, a total of 10 A will be going through the battery.

Imagine you are a battery. You can't see that you have two resistors. What does it feel like to you? $\frac{V}{I} = R$, and V = 12 and I = 10. So the effective resistance of the two resistors in parallel is $\frac{12}{10}$ or $\frac{6}{5}\Omega$.

Resistance in Parallel

If you have several resistances R_1, R_2, \ldots, R_n wired in parallel, their effective resistance R_t is given by

$$\frac{1}{R_t}=\frac{1}{R_1}+\frac{1}{R_2}+\ldots+\frac{1}{R_n}$$

In our example:

$$\frac{1}{R_t} = \frac{1}{2} + \frac{1}{3} = \frac{5}{6}$$

Thus $R_t = \frac{6}{5}\Omega$.

Exercise 3 Resistors In Parallel

Working Space

What is the current going through the battery? What is the drop over the 4Ω resistor? What is the current in each branch?



This is a draft chapter from the Kontinua Project. Please see our website (https://kontinua. org/) for more details.

APPENDIX A

Answers to Exercises

Answer to Exercise 1 (on page 1)

V = IR so $I = \frac{V}{R} = \frac{24V}{6\Omega} = 4A$.

Answer to Exercise ?? (on page 3)

There is a total resistance of 8Ω , so your 16V will push 2A of current around the circuit.

2A going through a 5 Ω resistor represents a 10V drop.

2A going through a 3Ω resitor represents a 6V drop.

Answer to Exercise 3 (on page 5)

The effective resistance of the 6Ω and the 3Ω is 2Ω because

$$\frac{1}{R_{T}} = \frac{1}{6} + \frac{1}{3} = = \frac{1}{2}$$

So the battery experiences a resistance of $4\Omega + 2\Omega = 6\Omega$. A 12V will push 2A through a resistance of 6Ω .

The voltage drop across the 4 Ω resistor is 2A × 4 Ω = 8V. Thus there will be a 4V drop across the two resistors in parallel. So 2/3 A will flow through the 6 Ω resistor. 4/3 A will flow through the 3 Ω resistor.





INDEX

Kirchhoff's voltage law, 2

resistance in parallel, 4